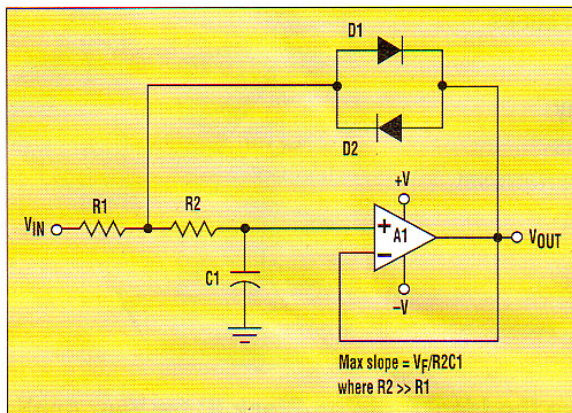



Special Low – Pass Filter Limits Slope

Adding several components to a simple first-order; low-pass filter; helps to create a different yet handy filter. The circuit shown in Figure 1 combines a low-pass filter (R2, C1, A1) with a bidirectional diode clipping network (R1, D1, D2). The result is a filter that will limit the maximum slope (not frequency) it passes.

Typical uses for this circuit are shown in Figure 2a-2d. in general, it's used to create ramps from step voltages, generate triangle/trapezoid waveforms from square waves, remove unwanted fast components (noise/transient) from any signal, or limit the maximum rate of change of any signal.



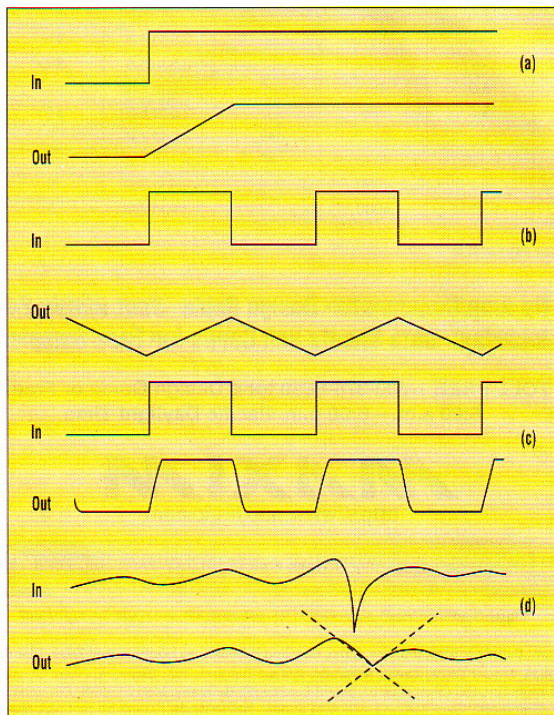1. Combining a low-pass filter with a bidirectional clipping network, this filter can limit the maximum slope (not frequency) that it will pass.



2. Typical uses for the filter include: (a) creating ramps from step voltages; (b) generating triangle waveforms or (c) trapezoid waveforms from square waves; and (d) limiting the maximum rate of change of any signal.

Here's how it works. Whenever the input voltage V_{IN} differs from the output voltage V_{OUT} by one forward diode drop or more, one of the diodes will turn on ($D1$ when $V_{IN} > V_{OUT}$ and $D2$ when $V_{IN} < V_{OUT}$). When this happens, the voltage across $R2$ is held fairly constant (because the voltage at the “+” input and the output of $A1$ are equal) at one forward diode drop.

With a fixed voltage across $R2$ and, therefore, a constant current through it, the capacitor $C1$ charges linearly in stead of exponentially. The maximum slope (V/T) that the circuit will pass is equal to the V_F of the diodes used divided by $R2C1$ (maximum slope (V/T) = $V_F / R2C1$). This assumes $R2 \gg R1$. No matter how quickly the input voltage changes, the output will never change any faster than the limit set by $R2C1$. any signal or part of a signal with a slope less than this limit simply passes through the circuit unaffected.

V_{IN} should be driven by a low impedance source. Resistor $R1$ limits the current through $D1$ or $D2$ when they conduct. Typically $R1$ is 1k-10k. its value should be kept as small as practical and depends on the drive

capabilities of A1 and the op-amp or other device driving V_{IN} . R2's resistance should be much greater than that of R1 to swamp out its contribution to the circuit's R2C1 time constant. R2 and C1 form a low-pass filter and A1 buffers it and provides a low impedance path for D1 or D2 when in conduction. For the best performance, D1 and D2 should be low V_F (Schottky) types, although other diode types (1N914, 1N4148, etc) will work satisfactorily.

When a square wave or step voltage is slope-limited by this circuit, a slight rounding will be seen at the top and bottom of the output waveform. This is due to the loss of overhead voltage (needed for diode conduction) that occurs when the capacitor has charged within one diode drop of the input's peak voltage. This rounding is minimized by using low V_F diodes, keeping R1 as small as possible, and by using the largest amplitude input waveform your supply voltage will allow.

I originally came up with this circuit while designing a servo control loop. I needed a simple way to limit the rate of change of the servo's output signal. It also can be used to soft start lights, create smooth motor speed transitions, filter a signal by its slope instead of its frequency, tame ill-behaved servo circuits, slow square wave transitions (without excessive rounding), and so on. Unlike integrator-based circuits this circuit works with single-ended or bidirectional supplies.